1. Construct a truth table for the following:

a.
$$(x + y)(x + z)(x' + z)$$

<u>Ans</u>

| X | y | Z | x' | x + y | x + z | x' + z | (x+y)(x+z)(x+z) |
|---|---|---|----|-------|-------|--------|-----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |

2. Show that x = xy + xy'

a. Using truth tables

| X | y | y' | xy | xy' | xy + xy' |
|---|---|----|----|-----|----------|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 |

b. Using Boolean identities

$$x = xy + xy' = x(y+y') \# Distributive Law$$

= $x(1) \# Inverse Law$
= $x \# Identity Law$

$$\underline{\mathbf{Ans}} : \mathbf{x} = \mathbf{xy} + \mathbf{xy'}$$

2. Given the function: F(x,y,z) = xy'z + x'y'z + xyz


a. List the truth table for F.

Ans

| X | у | Z | x' | y' | xyz | xy'z | x'y'z | xy'z + x'y'z + xyz |
|---|---|---|----|----|-----|------|-------|--------------------|
| 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |

b. Draw the logic diagram using the original Boolean expression

<u>Ans</u>

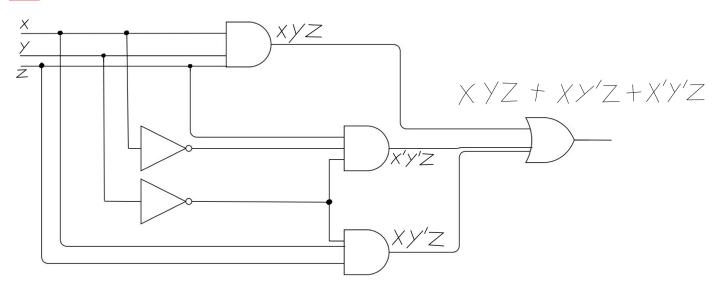

c. Simplify the expression using Boolean algebra and identities.

Ans

$$F(x,y,z) = xy'z + x'y'z + xyz \# Idempotent Law$$

$$= z(xy' + x'y' + xy) \# Distributive Law$$

$$= z(x(y + y') + x'y') \# Commutative \& Distributive Laws$$

$$= z(x(1) + x'y') \# Inverse Law$$

$$= z(x + x'y') \# Identity Law$$

$$= z((x + x')(x + y')) \# Distributive Law$$

$$= z((1)(x + y')) \# Inverse Law$$

$$= z(x + y') \# Identity Law$$

$$= xz + y'z \# Distributive Law$$

d. Simplify the expression using KMap

Ans

| x \\ yz | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |

$$xy'z$$
 $xy'z$


e. List the truth table for your answer in Part d.

<u>Ans</u>

| X | У | Z | y' | XZ | y'z | y'z + xz |
|---|---|---|----|----|-----|----------|
| 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 |

f. Draw the logic diagram for the simplified expression in Part d.

<u>Ans</u>

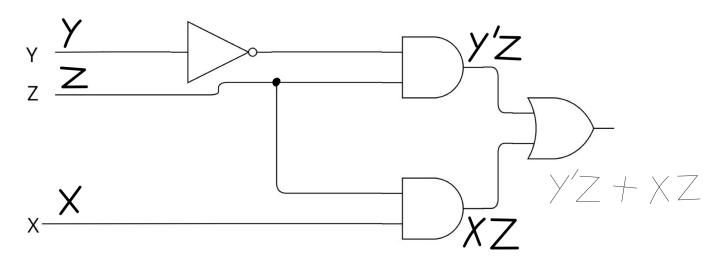

Group 2 (8 people)

- 1. 65130500201 Kampol Suwannatam
- **2**. 65130500204 Jirawat Rongsupan
- **3**. 65130500207 Chewin Grerasitsirt
- 4. 65130500209 Natthanon Somroop
- 5. 65130500210 Nontakorn Chatkoonsathien
- 6. 65130500212 Nithit Lertcharoensombat
- 7. 65130500227 Issadaorn Kulsantao
- 8. 65130500237 Chayapol Mahatthanachai