


1. How many inputs does a decoder have if it has 64 outputs?

Ans 6

2. How many control lines does a multiplexer have if it has 32 inputs?

Ans 5

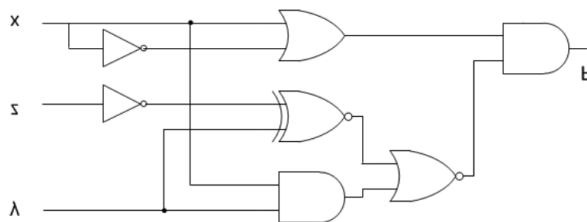
3. Find the truth table that describes the following circuit:



Ans

x	y	z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

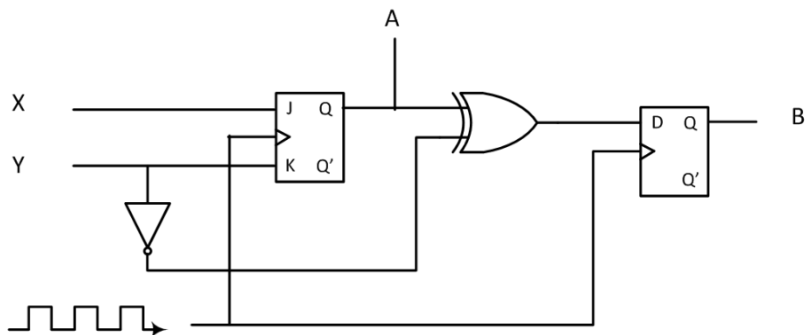4. Complete the truth table for the following sequential circuit:



Ans

X	Y	A	Next State	
			A	B
0	0	0	0	1
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

For B				Current	Next state
X	Y	A	Y'	A XOR Y'	B (D)
0	0	0	1	1	1
0	0	1	1	0	0
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	1	1	1
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1

For A		Current	Next state
X	Y	A	JK(X Y)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

5. 59. A Mux-Not flip-flop (MN flip-flop) behaves as follows: If $M = 1$, the flip-flop complements the current state. If $M = 0$, the next state of the flip-flop is equal to the value of N .

1. a) Derive the characteristic table for the flip-flop.
2. b) Show how a JK flip-flop can be converted to a MN flip-flop by adding gate(s) and inverter(s).

Ans.

- a) The characteristic table for the MN flip-flop:

M	N	Q(t+1)
0	0	0
0	1	1
1	0	Q'(t)
1	1	Q'(t)

- b) To convert a JK flip-flop to an MN flip-flop, we must express J and K in terms of M and N, as follows (remember with a JK flip-flop, 01 as input means reset, 10 means set, 00 means no change, and 11 means toggle):

M	N	J	K
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	1

From the above we can see that J is $M + N$ and K is $M + N'$. So we have:

